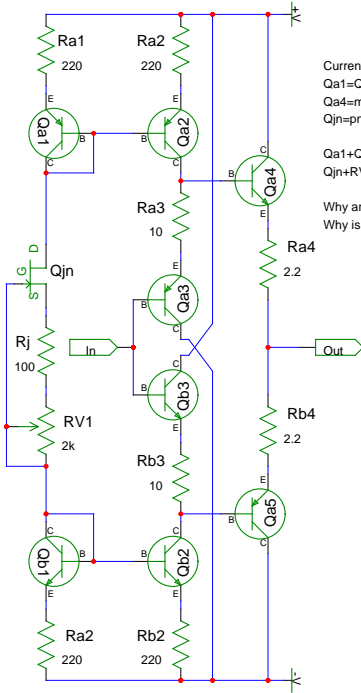


## Transistor Amplifiers (3)


2008-07-24




**Current Boosted Output**  
 $Qa1=Qa2=Qa3=2n5087$ ,  $Qb1=Qb2=Qb3=2n5088$   
 $Qa4=mje243$  or  $bd139$ ,  $Qb4=mje253$  or  $bd140$   
 $Qjn=pn4392$

$Qa1+Qb1$  are wired in diode mode to match their current mirrors.  
 $Qjn+RV1$  seems to fine tune the bias.

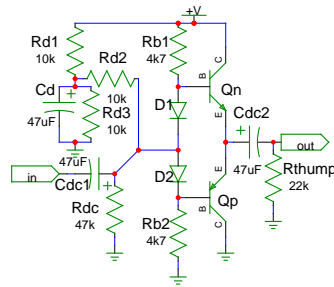
Why are the middle transistors crossed?  
 Why is this a 3-layer instead of the usual 2?



**Single Supply Rail Booster.**  
 $Cd+Rd^*$  form a voltage divider to raise the signal to half of  $V_{supply}$ .  
 $Cdc1+Rdc$  form a high pass filter and should be chosen carefully.  
 Watch polarity of  $Cdc1$  if DC is on the signal (electric mic).  
 $Cdc2+Rthump$  also form a high pass filter.  
 $Rthump$  will remove the DC off the capacitor to avoid plug in thumps.  
 Since electrolytics don't have a very good phase response, they can also be bypassed with a good film capacitor.

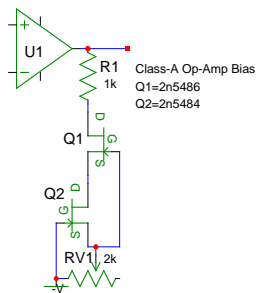


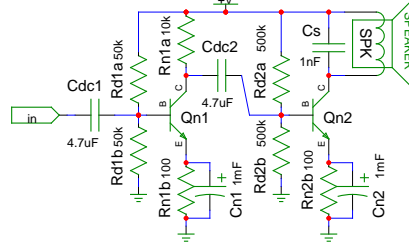**Class-A Op-Amp Bias**  
 $Q1=2n5486$   
 $Q2=2n5484$




**Transistor Amplifier (Single Rail, Class A Inverting).**  
 Interesting design. Unsure if it will really work.  
 Seems to have maximum gain.  
 Change  $Rd^*$  to 2/3 splits depending on  $V_{supply}$ ?

### Discrete Headphone Amp

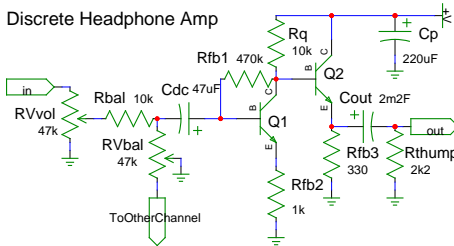

**Headphone Amplifier, Class A, Single Supply Rail, Inverted.**  
 Circuit is designed to be self biasing. Circuit works 6-20v.  
 Single channel shown. Duplicate it for stereo.  
 $RV_{vol}$  is volume control and is a dual gang pot for stereo.  
 $R_{bal}$  provides minimum resistance for the balance control so signal isn't shorted to ground.  
 $RV_{bal}$  is balance control and connects to the same spot on the other channel.  
 $Cdc$  blocks DC on the input signal. Watch polarity if DC is on the signal (electret mics).  
 $Q1=Q2=bc549c$  ( $V_{ce}=V_{cb}=30v$ ,  $V_{eb}=5v$ ,  $100mA$ ).  
 $Q1$  provides an inverting amplifier.  $Q2$  is the output buffer. Gain will be less than 10 as shown.  
 $R_{thump}$  takes the DC out of  $C_{out}$  and prevents thumps when the headphones are plugged in.

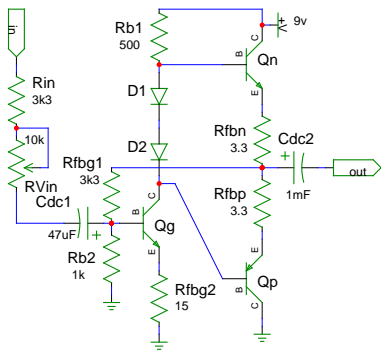

**Transistor Radio Amp (Class B Inverted, 50mW estimated, 30mA from 9v battery)**  
 This is a somewhat temperamental design, so component values need to be close.  
 As with all amps like this, power rails need to be very clean to avoid adding output noise.  
 Input impedance is about 500ohms. Gain is about 5x with 8ohm speaker.  $V_{p-p}$  is about 4v.  
 $R_{in}$  could only be a pot but will have distortion problems below 3k3.  
 If the signal in voltage is too high, add a 10k pot volume control before  $R_{in}$ .  
 Watch polarity of  $Cdc1$  if DC is on the signal (electret mic).  
 $Cdc1$  and  $Cdc2$ . Watch out for RC filter calcs. A good film cap may be paralleled for better phasing.  
 $R_{fbg1}$  may be a pot for variable gain.  
 $NPNs=2n3053$ ,  $2n2222$ .  $PNP=2n2905$ ,  $2n4403$ .  
 $D1+D2$  bias  $Qn+Qp$  into conduction. Zeners could be used here for higher voltage drop.  
 The  $R_{fbn}+R_{fbp}$  resistors bias the voltage equally across  $Qn+Qp$ . They should be well matched.  
 When bias current increases, voltage between emitter and base decrease, reducing conduction.  
 General limits for 9v supply:  $R_{in}>3k3$ ,  $R_{b1}=500-1k$ ,  $R_{fbg1}<3k3$ .

As the positive signal swing reaches a maximum, the voltage drop across  $R_{b1}$  decreases and reduces the base current to  $Qn$ . This avoids the signal from going all the way to the rail and causes a soft distortion.

Question: Is  $R_{b2}$  really needed? Better impedance and signal level if removed.